

**Lab 1 - SIMON encryption/decryption**

Joseph Burke

Idan G. Kanter

Seth Rausch

ECE 459 - Secure & Trustworthy Computer Hardware Design

Spring 2017

Dr. Garrett S. Rose

January 28 2017

Instructor Signature: \_\_\_\_\_

**Abstract/Introduction**

The field of security in software and hardware was always an important subject. A few encryption algorithms were introduced including the older Data Encryption Standard (DES), and the newer Advanced Encryption Standard (AES). AES is a very strong non-Feistel encryption algorithm; however, it is also considered heavyweight; AES requires heavy usage of the system resources as memory, area, and power. Due to the rising need of a more lightweight encryption algorithm for FPGAs, ASICs, Internet of Things (IOT), embedded systems, and more, a team at the National Security Agency (NSA) introduced the SIMON block cipher algorithm which is optimized for hardware. SIMON is a Feistel encryption algorithm that uses less system resources than the AES, which makes it suitable for small systems that were introduced above.

The purpose of the lab is to learn how SIMON works and to implement some of its functions. After reading two papers about the implementation of SIMON, the round and the key expansion function are implemented. After the algorithm is completed, some test benches are run to simulate the encryption. Next, the program is synthesized, implemented, and is generated to a bit file for testing on a Nexys-4 FPGA board. Finally, the implementation is programmed to the board and the program encrypts two image files. In addition, the FPGA is used to test the decryption of the images since SIMON is a Feistel algorithm. During the whole process, interesting features, observations, and shortcomings of SIMON are recorded.

Simon is comprised of several round functions that do various different operations on the plaintext for encryption. These operations are comprised of bitwise XOR, bitwise AND, and left circular shift. When the plaintext is put into the round function the block data is split into 2 halves and at the end of each round the left and right halves of the data are swapped.

 


Figure. 1.

Figure 1 shows the SIMON round function which is used for encryption and its inverse for decryption. We define the SIMON round function used for encryption as:

$$R(l, r, k) = ((S^1(l) \& S^8(l)) \oplus S^2(l) \oplus r \oplus k, l)$$

and the SIMON round function used for decryption as:

$$R^{-1}(l, r, k) = (r, (S^1(r) \& S^8(r)) \oplus S^2(r) \oplus l \oplus k)$$

Additionally, the SIMON key schedule allows us to use key expansion which generates all the round keys from the master keys. This is done in each round  $i$ , by combining the current cached previous  $n$  round keys with the constant  $c$  and a 1-bit round constant. Key expansion utilizes bitwise XOR ( $x \oplus y$ ) and right bitwise rotation (ROR). The SIMON four word key expansion is shown in figure 2. The key expansion function can be expressed as:

$$K_i(k, c, z_j) = F(k_{i+3}, k_{i+1}) \oplus S^{-1}(F(k_{i+3}, k_{i+1})) \oplus k_i \oplus c \oplus (z_j)_i$$

$$F(x, y) = S^{-3}(x) \oplus y$$






$$F(x, y) = S^{-3}(x) \oplus y$$






The diagram illustrates the key schedule for the Camellia cipher. It starts with a 64-bit master key, which is split into four 16-bit words: `key_word(63:48)`, `key_word(47:32)`, `key_word(31:16)`, and `key_word(15:0)`. These words are processed through a series of operations to derive the round keys. The operations include rotations (e.g., `shift_rt3`, `shift_rt1`) and XORs (e.g., `xor01`, `xor02`, `xor4`). The final round keys are `uout0`, `uout1`, and `uout2`. The diagram also includes labels for specific operations: `bambam`, `wilma`, and `fred`.


In figure 3 we see that it is very similar to figure 2. This is the key expansion with our vhd1 components. Each arrow is a different signal in vhd1. Finally, the signals are port mapped to tell the fpga where the signals are traveling to and from each component.

In the behavioral simulation we showed that the 64 bit passed plaintext was successfully encrypted by the key. As you can see the ctext line is the cipher text which is alternating at each

round.

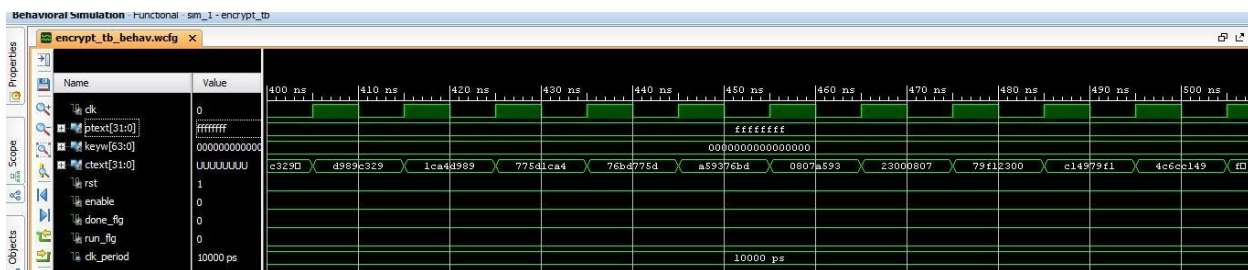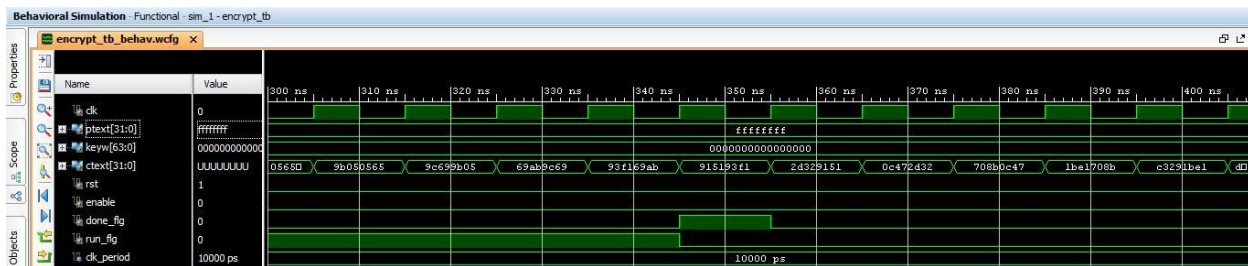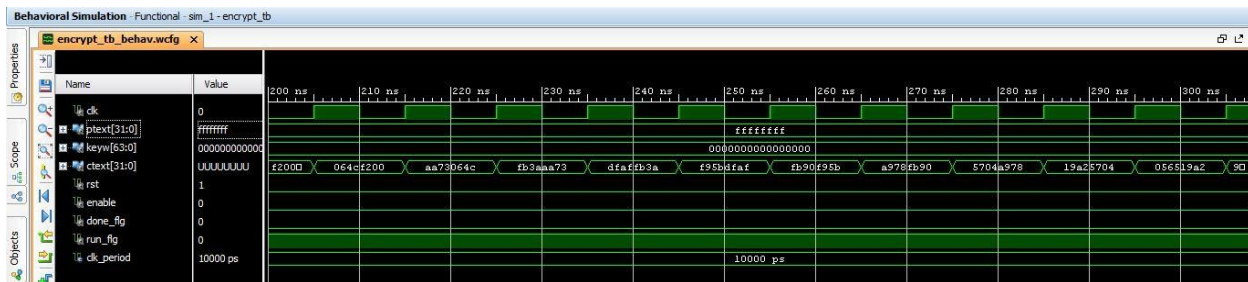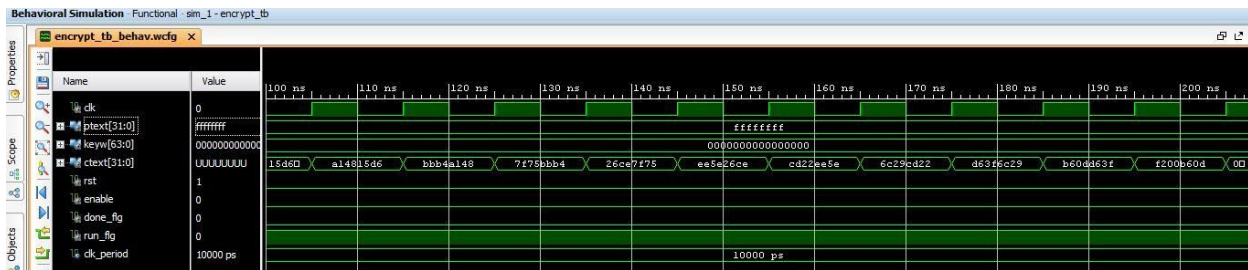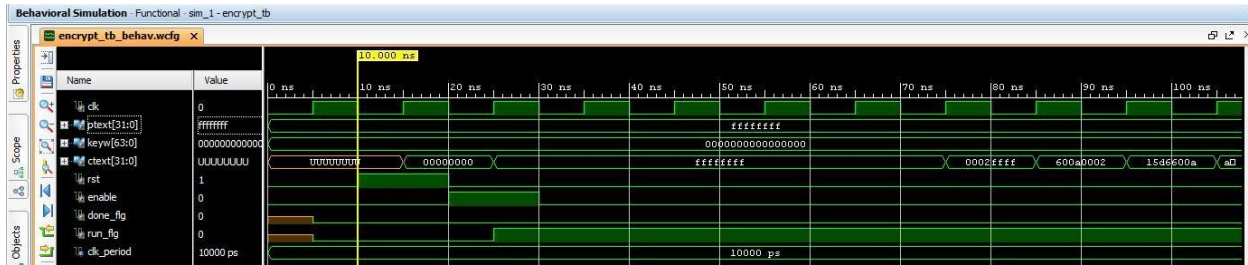

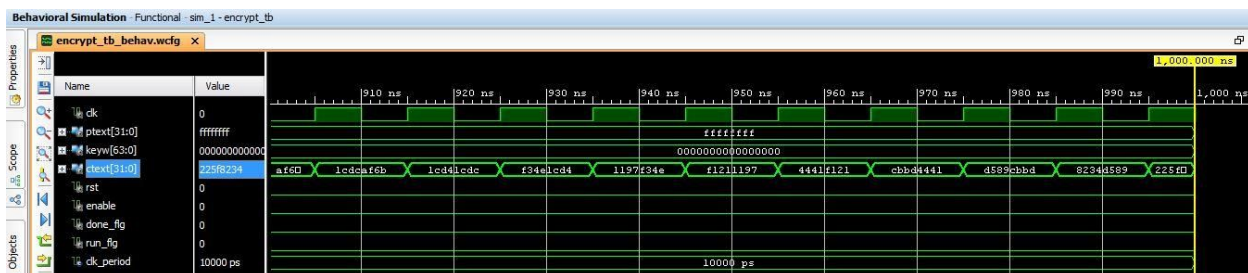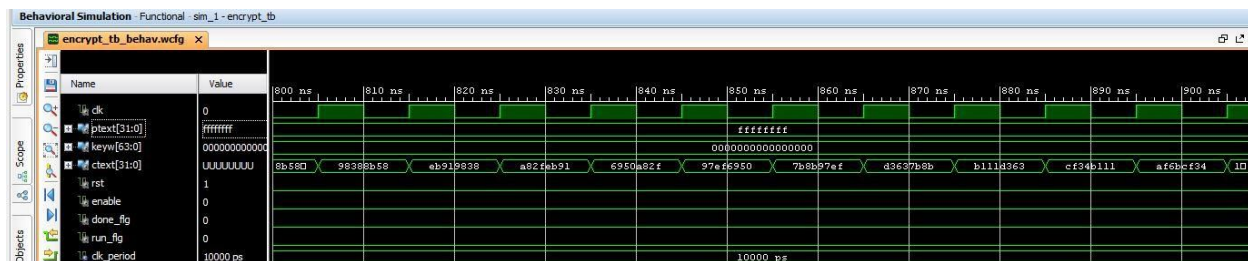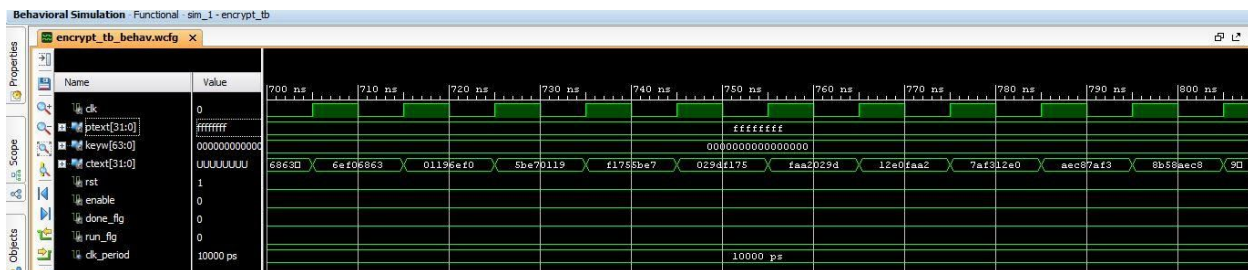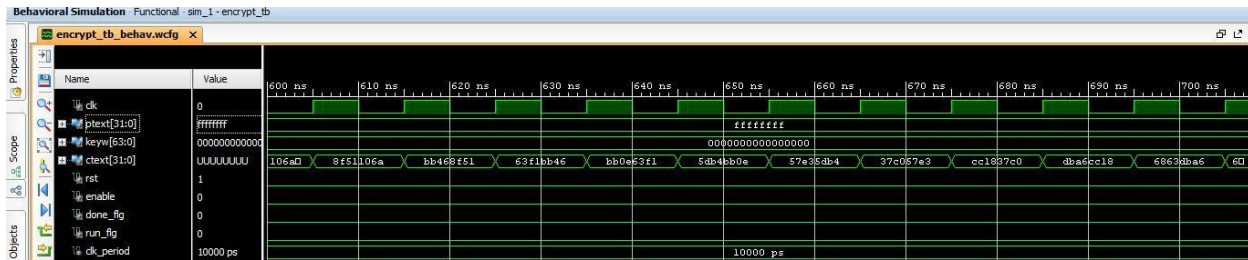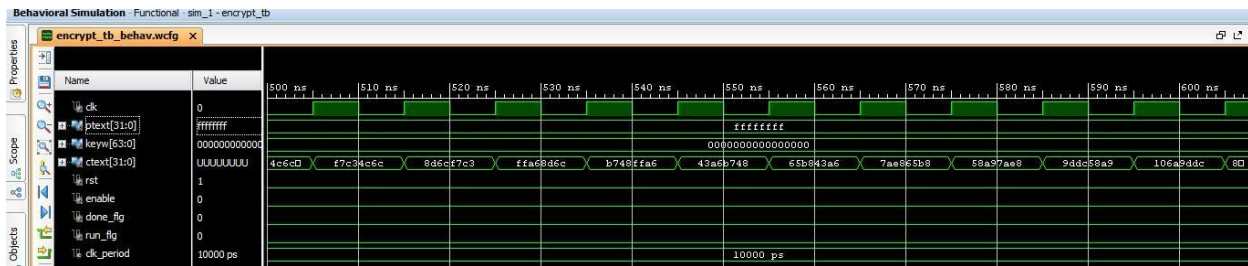

 **Figure 1 - Payton\_encrypt****Figure 2 - PowetT\_encrypt**

## Observations

On inspection of the encrypted PGM files depicted in figures 1 and 2 you can see that the SIMON cipher works well in some cases and not so well in others. In figure 2 it is evident that the image was not very well encrypted, as the pattern is still visible. This shows some of the limitations and places where it could be improved. We found that SIMON64/128 has many tradeoffs that come with the design as well as the issues we encountered during the implementation. The SIMON family of block ciphers has proved to be a great candidate for applications that require flexible, lightweight cryptography.

## Appendix

### Round\_Cipher.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.all;

use IEEE.STD_LOGIC_ARITH.all;

use IEEE.STD_LOGIC_UNSIGNED.all;

entity round_cipher is

    port (

        blockcipher : in  std_logic_vector(31 downto 0);

        key_word      : in  std_logic_vector(15 downto 0);

        cipher_text   : out std_logic_vector(31 downto 0)

    );

end round_cipher;
```

```
architecture your_code of round_cipher is

    -- You can use these components if needed...

    -- Feel free to develop your own logic as well...
```

```
component shift_left1 is

    port (

        input1 : in  std_logic_vector(15 downto 0);

        output  : out std_logic_vector(15 downto 0)

    );

end component shift_left1;
```

```
component shift_left2 is

    port (

        input1 : in  std_logic_vector(15 downto 0);

        output  : out std_logic_vector(15 downto 0)
```



```
);  
end component shift_left2;  
  
component shift_left8 is  
  port (  
    input1 : in  std_logic_vector(15 downto 0);  
    output  : out std_logic_vector(15 downto 0)  
  );  
end component shift_left8;  
  
component xor16bit is  
  port (  
    input1 : in  std_logic_vector(15 downto 0);  
    input2 : in  std_logic_vector(15 downto 0);  
    output  : out std_logic_vector(15 downto 0)  
  );  
end component xor16bit;  
  
component and16bit is  
  port (  
    A : in  std_logic_vector(15 downto 0);  
    B : in  std_logic_vector(15 downto 0);  
    Y : out std_logic_vector(15 downto 0)  
  );  
end component and16bit;  
  
component ctext_reg is  
  port (  

```

```

    clk          : in  std_logic;
    reset        : in  std_logic;
    round        : in  std_logic_vector(7 downto 0);
    input1_16bits : in  std_logic_vector(15 downto 0);
    input2_16bits : in  std_logic_vector(15 downto 0);
    flop32       : out std_logic_vector(31 downto 0);
    text_flag    : out std_logic
);
end component ctext_reg;

-- Will need to declare intermediary signals

    signal left_shift_1_block : std_logic_vector (15 downto 0);           -- upper block
after left shift by 1 bit

    signal left_shift_2_block : std_logic_vector (15 downto 0);           -- upper block
after left shift by 2 bit

    signal left_shift_8_block : std_logic_vector (15 downto 0);           -- upper block
after left shift by 8 bit

    signal and_1_8_blocks     : std_logic_vector (15 downto 0);           -- AND of the
1 and 8 left shifts

    signal and_XOR_lower      : std_logic_vector (15 downto 0);           -- XOR of and
result with lower_block

    signal sl2_XOR_xor1       : std_logic_vector (15 downto 0);           -- XOR of the
left shift by 2 block with the upper xor

    signal lower_block        : std_logic_vector (15 downto 0);           -- lower block
of blockcipher

    signal upper_block        : std_logic_vector (15 downto 0);           -- upper block
of blockcipher

    signal xor2_XOR_key       : std_logic_vector (15 downto 0);           -- xor of

```

middle xor and the key

```
begin

    s11      :  shift_left1 port map (blockcipher(31 downto 16), left_shift_1_block);
-- upper block shift left by 1

    s18      :  shift_left8 port map (blockcipher(31 downto 16), left_shift_8_block);
-- upper block shift left by 8

    and_1_8   :  and16bit   port map (left_shift_1_block, left_shift_8_block,
and_1_8_blocks);    -- AND the 1-bit left shift and the 8-bit left shift blocks

    s12      :  shift_left2 port map (blockcipher(31 downto 16), left_shift_2_block);
-- upper block shift left by 2

    xor1      :  xor16bit   port map (and_1_8_blocks, blockcipher(15 downto 0),
and_XOR_lower);    -- XOR the result of the AND operation with the lower block of the
blockcipher

    xor2      :  xor16bit   port map (left_shift_2_block, and_XOR_lower, s12_XOR_xor1);
-- XOR the result of upper xor with the 2-bit left shift block

    xor3      :  xor16bit   port map (s12_XOR_xor1, key_word, xor2_XOR_key);
-- XOR the result of middle xor with the key

    lower_block <= blockcipher(31 downto 16);    -- new lower block is the upper block

    upper_block <= xor2_XOR_key;                -- new upper block is the result of
bottom xor

    cipher_text <= upper_block & lower_block;    -- attach the two blocks together to form
the cipher text - output

end your_code;
```

KEY\_EXPANSION.vhd

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.std_logic_signed.all;

entity key_expansion is

    port (

        round      : IN  std_logic_vector(7 downto 0);

        sel        : IN  std_logic;

        key_word    : IN  std_logic_vector(63 downto 0);

        clk        : IN  std_logic;

        reset       : IN  std_logic;

        key_expansion : OUT std_logic_vector(15 downto 0)

    );

end key_expansion;

architecture your_code of key_expansion is

    -- These components are available to use if desired...

    -- Feel free to implement your own...

    component reg16 is

        port (

            clk      : in  std_logic;

            reset    : in  std_logic;

            input_16bits : in  std_logic_vector(15 downto 0);

            flop16    : out std_logic_vector(15 downto 0)

        );

    end component reg16;
```

```
component mux2to1 is
```

```
  port (
```

```
    SEL : in  std_logic;
```

```
    A   : in  std_logic_vector (15 downto 0);
```

```
    B   : in  std_logic_vector (15 downto 0);
```

```
    X   : out std_logic_vector (15 downto 0)
```

```
  );
```

```
end component mux2to1;
```

```
component shift_right1 is
```

```
  port (
```

```
    input1 : in  std_logic_vector(15 downto 0);
```

```
    output : out std_logic_vector(15 downto 0)
```

```
  );
```

```
end component shift_right1;
```

```
component shift_right3 is
```

```
  port (
```

```
    input1 : in  std_logic_vector(15 downto 0);
```

```
    output : out std_logic_vector(15 downto 0)
```

```
  );
```

```
end component shift_right3;
```

```
component xor16bit is
```

```
  port (
```

```
    input1 : in  std_logic_vector(15 downto 0);
```

```
    input2 : in  std_logic_vector(15 downto 0);
```

```
    output : out std_logic_vector(15 downto 0)
```

```

    );

end component xor16bit;

component u_bit is
    port (
        round : in  std_logic_vector(7 downto 0);
        u_out  : out std_logic_vector(15 downto 0);
        u_int  : out std_logic_vector(15 downto 0)
    );
end component u_bit;

component xor16bit_triple is
    port (
        input1 : in  std_logic_vector(15 downto 0);
        input2 : in  std_logic_vector(15 downto 0);
        input3 : in  std_logic_vector(15 downto 0);
        input4 : in  std_logic_vector(15 downto 0);
        output  : out std_logic_vector(15 downto 0)
    );
end component xor16bit_triple;

-- Will need to declare intermediary signals here
    signal uout0      :      std_logic_vector(15 downto 0);      -- 'C'
    signal uout1      :      std_logic_vector(15 downto 0);      -- 'Z'
    signal XOR4_out    :      std_logic_vector(15 downto 0);      -- output of
XOR 'C', 'Z', key0, XOR2_out - "bambam"
    signal mux1_out    :      std_logic_vector(15 downto 0);      -- output of
left mux1

```

```

    signal mux2_out          :      std_logic_vector(15 downto 0); -- output of 2nd
from the left mux2

    signal mux3_out          :      std_logic_vector(15 downto 0); -- output of 3rd
from the left mux3

    signal mux4_out          :      std_logic_vector(15 downto 0); -- output of right
mux4

    signal key3              :      std_logic_vector(15 downto 0);      -- output of
register key3

    signal key2              :      std_logic_vector(15 downto 0);      -- output of
register key2

    signal key1              :      std_logic_vector(15 downto 0);      -- output of
register key1

    signal key0              :      std_logic_vector(15 downto 0);      -- output of
register key0 - "fred"

    signal sr3_out           :      std_logic_vector(15 downto 0);      -- output of the
shift_rt3

    signal key1_XOR_sr3      :      std_logic_vector(15 downto 0);      -- output of xor01,
input are key1 and sr3

    signal sr1_out           :      std_logic_vector(15 downto 0);      -- output of the
shift_rt1

    signal xor2_out          :      std_logic_vector(15 downto 0);      -- output of
xor2_out - "Wilma"

begin

    u_find      :      u_bit      port map (round, uout0, uout1);

                                -- round -> 'C' and 'Z'

    xor4        :      xor16bit_triple      port map (uout0, uout1, key0, xor2_out,

```

```

XOR4_out);          -- xor 4 inputs -> input of mux1

    mux1      :      mux2to1      port map (sel, key_word(63 downto 48),
XOR4_out, mux1_out); -- mux xor4_output and key -> key3

    key3_reg   :      reg16      port map (clk, reset, mux1_out, key3);
    -- register 3

    mux2      :      mux2to1      port map (sel, key_word(47 downto 32),
key3, mux2_out);    -- mux key3 and key -> key2

    key2_reg   :      reg16      port map (clk, reset, mux2_out, key2);
    -- register 2

    sr3       :      shift_right3 port map (key3, sr3_out);
    -- key3 shift right by 3 bits

    mux3      :      mux2to1      port map (sel, key_word(31 downto 16),
key2, mux3_out);    -- mux key2 and key -> key1

    key1_reg   :      reg16      port map (clk, reset, mux3_out, key1);
    -- register 1

    mux4      :      mux2to1      port map (sel, key_word(15 downto 0), key1,
mux4_out);          -- mux key1 and key -> key0

    key0_reg   :      reg16      port map (clk, reset, mux4_out, key0);
    -- register 0

    xor1      :      xor16bit     port map (key1, sr3_out, key1_XOR_sr3);
    -- xor key1 and shift_rt3

    sr1       :      shift_right1 port map (key1_XOR_sr3, sr1_out);
    -- xor01 shift right by 1 bit

    xor2      :      xor16bit     port map (sr1_out, key1_XOR_sr3, xor2_out);
    -- xor shift_rt1 and xor01

    key_expansion <= key0;      -- output

```



```
end your_code;
```