

ECE 459/559

Secure & Trustworthy

Computer Hardware Design

VHDL Review

Garrett S. Rose
Spring 2017

Summary

- Brief overview of VHDL
 - Behavioral VHDL
 - Structural VHDL
- Simple examples with VHDL
- Some VHDL for SIMON encryption

Some History of VHDL


VHSIC Hardware Description Language

- U.S. government (Dept. of Defense) initiative
 - Wanted better, concise documentation of behavior
- VHDL syntax borrows heavily from Ada (DoD requirement)
- Initial VHDL version: IEEE 1076-1987
- Standard types included in library IEEE 1164
- IEEE 1076 updated in 1993
- A few minor updates (mostly modeling) in 2000 and 2002

VHDL is an Entity-based Language

- Entity: a unit in digital system design
- An entity describes **name** of unit, its **ports**, and **types** and **directions** of those ports
 - Port: an input or output of the design entity
 - Communication with other entities via ports
- Example:
 
```
entity my_circuit is
  port(
    a : in  std_logic;
    b : in  std_logic;
    c : out std_logic);
end my_circuit;
```




Signal Values

- IEEE 1164 standard defines nine values for digital **signal**:
 - 1: logic value 1
 - 0: logic value 0
 - U: uninitialized
 - Z: high impedance
 - X: forcing unknown
 - W: weak unknown
 - L: weak 0
 - H: weak 1
 - "-": don't care


Port Mode

 - Identifies direction of data flow through the port
- All ports must have an identified mode:



Port Example

 
```
entity dumb_circuit is
  port( in1, in2, in3 : in  std_logic;
        out1, out2    : out std_logic);
end dumb_circuit;
...
out1 <= in1 and in2;
out2 <= out1 or in3;
```



Port Example

```
entity dumb_circuit is
  port( in1, in2, in3 : in  std_logic;
        out1, out2    : out std_logic);
end dumb_circuit;
...
out1 <= in1 and in2;
out2 <= out1 or in3;
```

 out1 is being “read”
– this is not allowed!



- This is where mode “buffer” is useful
 - If out1 were declared in entity as “buffer” instead of “out,” there would be no error
 - May cause other problems → try to avoid use of buffer mode

IEEE Array/Vector Type: `std_logic_vector`

- `std_logic_vector` is simply an array where each element is of type `std_logic` (one bit)

```
entity mux2x8 is
    port( bus_a    : in  std_logic_vector(7 downto 0);
          bus_b    : in  std_logic_vector(7 downto 0);
          sel      : in  std_logic;
          bus_out   : out std_logic_vector(7 downto 0));
end mux2x8;
```

- In the *architecture*, individual bits can be referred to:

```
bus_out(7) <= bus_a(7) when sel = '0' else bus_b(7);
```


- The whole bus can be assigned with a bitstring:

```
bus_out <= "11110000";
```

Architecture

- The entity declares the device and describes the I/O
- The architecture describes what the device does and is


```
architecture my_architecture_name of my_circuit is  
    -- declarative section  
begin  
    -- activity statements or architecture body  
end my_architecture_name;
```



Refers to a previously
declared entity

Entity & Architecture Together

 - Each entity can have multiple architectures




```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
entity my_circuit is  
    port( a, b : in std_logic;  
          c, d : out std_logic);  
end my_circuit;
```

```
architecture behav of my_circuit is  
    signal andab : std_logic;  
begin  
    -- these are CONCURRENT statements  
    c <= andab;  
    d <= not andab;  
    andab <= a and b;  
end behav;
```

Entity & Architecture Together

 - Each entity can have multiple architectures



Library declarations required to use IEEE standard library


```
library IEEE;
use IEEE.std_logic_1164.all;
```

```
entity my_circuit is
    port( a, b : in std_logic;
          c, d : out std_logic);
end my_circuit;
```

```
architecture behav of my_circuit is
    signal andab : std_logic;
begin
    -- these are CONCURRENT statements
    c <= andab;
    d <= not andab;
    andab <= a and b;
end behav;
```

Entity & Architecture Together

 - Each entity can have multiple architectures



Entity declaration defines the outer “black box” view of the design


```
library IEEE;
use IEEE.std_logic_1164.all;
```

```
entity my_circuit is
    port( a, b : in std_logic;
          c, d : out std_logic);
end my_circuit;
```

```
architecture behav of my_circuit is
    signal andab : std_logic;
begin
    -- these are CONCURRENT statements
    c <= andab;
    d <= not andab;
    andab <= a and b;
end behav;
```

Entity & Architecture Together

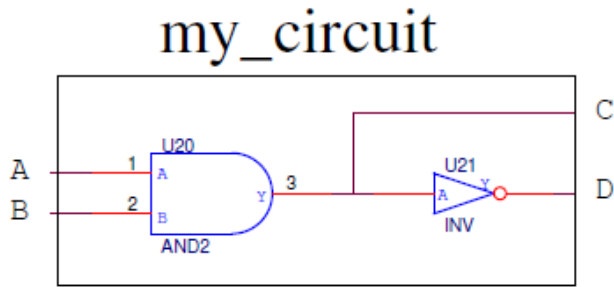- Each entity can have multiple architectures



Architecture is the main body of the design, describing the operation

Statements are concurrent


```
library IEEE;
use IEEE.std_logic_1164.all;

entity my_circuit is
    port( a, b : in  std_logic;
          c, d : out std_logic);
end my_circuit;
```

```
architecture behav of my_circuit is
    signal andab : std_logic;
begin
    -- these are CONCURRENT statements
    c <= andab;
    d <= not andab;
    andab <= a and b;
end behav;
```

Describing Architecture Practically

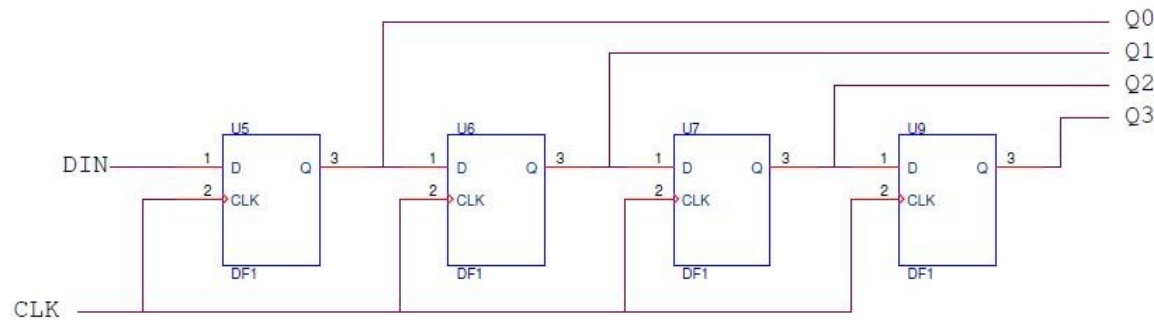- How should the architecture behave?
- Of what pieces is it composed and how are they connected
- The architecture is described by defining any needed subelements, how they behave and putting it all together



a 4-bit shift register

Describing Architecture Practically

4-bit Shift Register

- Define the design:
 - Inputs: DIN, CLK (need clock)
 - Outputs: 4 bits (`std_logic`) or 4-bit word (`std_logic_vector`)
- Behavior in English:
 - On rising edge of clock, shift DIN into LSB, LSB into 2nd position, 2nd position to 3rd, and 3rd position to MSB
 - “positions” must instantiate memory elements (e.g. flip-flops)

Describing Architecture Practically

4-bit Shift Register

```
library IEEE;
use IEEE.std_logic_1164.all;

entity shr_4b is
    port( DIN, CLK      : in  std_logic;
          Q0, Q1, Q2, Q3 : out std_logic);
end shr_4b;
```

Describing Architecture Practically

4-bit Shift Register – Behavioral

```
architecture behavioral of shr_4b is
begin
    storage: process is
        variable str_q0, str_q1, str_q2, str_q3 : std_logic;
    begin
        if CLK = '1' then
            str_q0 := DIN;
            str_q1 := str_q0;
            str_q2 := str_q1;
            str_q3 := str_q2;
        end if;
        Q0 <= str_q0 after 2 ns;
        Q1 <= str_q1 after 2 ns;
        Q2 <= str_q2 after 2 ns;
        Q3 <= str_q3 after 2 ns;
        wait on DIN, CLK;
    end process storage;
end behavioral;
```

Behavioral Architecture

- Abstract or algorithmic description – “high level”
- Structure is *not* defined specifically
- Usually contains:
 - **process** statements – can contain sequential statements
--may look more like software
 - **variable** declarations – for use in process
 - signal assignment statements
 - **wait** statements – temporarily suspends process, can model delay and timing

Describing Architecture Practically

4-bit Shift Register - Structural

- Need some additional, lower-level, entities

```
entity d_latch is  
  port( D, CLK : in  std_logic;  
        Q       : out std_logic);  
end entity d_latch;
```

```
architecture basic of d_latch is  
begin  
  dl_behav: process is  
    begin  
      if CLK = '1' then  
        Q <= D after 2 ns;  
      end if;  
      wait on DIN, CLK;  
    end process dl_behav;  
end basic;
```

Describing Architecture Practically

4-bit Shift Register - Refresher

```
library IEEE;
use IEEE.std_logic_1164.all;

entity shr_4b is
    port( DIN, CLK      : in  std_logic;
          Q0, Q1, Q2, Q3 : out std_logic);
end shr_4b;
```

Describing Architecture Practically

4-bit Shift Register - Structural

```
architecture structural of shr_4b is
    signal tmp_q0, tmp_q1, tmp_q2, tmp_q3 : std_logic;
begin
    bit0: entity work.d_latch(basic)
        port map(DIN, CLK, tmp_q0);
    bit1: entity work.d_latch(basic)
        port map(tmp_q0, CLK, tmp_q1);
    bit2: entity work.d_latch(basic)
        port map(tmp_q1, CLK, tmp_q2);
    bit3: entity work.d_latch(basic)
        port map(tmp_q2, CLK, tmp_q3);

    Q0 <= tmp_q0;
    Q1 <= tmp_q1;
    Q2 <= tmp_q2;
    Q3 <= tmp_q3;
end structural;
```

Structural Architecture

- Implements module as composition of subsystems
- Contains:
 - **signal** declarations for internal interconnections (wires)
--entity ports also treated as signals
 - Component instances of previously declared entity and architecture pairs for subsystems
 - **port maps** in component instances

SIMON Encryption in VHDL

(Lab 1 file: encrypt.vhd)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity encrypt is
  port ( clk           : in std_logic;
        reset          : in std_logic;
        key_word        : in std_logic_vector(63 downto 0);
        plain_text      : in std_logic_vector(31 downto 0);
        ENC_EN          : in std_logic;
        cipher_text     : out std_logic_vector(31 downto 0);
        done_flag       : out std_logic;
        running_flag    : out std_logic
    );
end encrypt;

...
```

I/O or external
interface for the part

SIMON Encryption in VHDL

(Lab 1 file: encrypt.vhd)

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.NUMERIC_STD.ALL;
```

```
entity encrypt is
```

```
    port ( clk           : in std_logic;  
          reset          : in std_logic;  
          key_word       : in std_logic_vector(63 downto 0);  
          plain_text     : in std_logic_vector(31 downto 0);  
          ENC_EN         : in std_logic;  
          cipher_text    : out std_logic_vector(31 downto 0);  
          done_flag      : out std_logic;  
          running_flag   : out std_logic
```

```
    );
```

```
end encrypt;
```

```
...
```

64-bit user
supplied key

32-bit block size
Input is plaintext

32-bit block size
output is ciphertext

SIMON Encryption in VHDL

Declarative Section

```

...
architecture Behavioral of encrypt is
  component round_cipher is
    port (
      blockcipher : in    std_logic_vector(31 downto 0);
      key_word    : in    std_logic_vector(15 downto 0);
      cipher_text : out   std_logic_vector(31 downto 0)
    );
  end component round_cipher;

```

Declare components to be used in design

```
...
signal block_half1, block_half2 : std_logic_vector(15 downto 0);
signal text_holder, temp_block : std_logic_vector(31 downto 0);
signal key_expanded : std_logic_vector(15 downto 0);
signal rnd : std_logic_vector(7 downto 0);
signal enc_run : std_logic;
```

Declare internal signals (wires between components)

begin

SIMON Encryption in VHDL

Main Architecture Body

Instantiate components
used in design

Use internal signals
to define connections

```
...
begin
    mux_left: mux2to1 port map(ENC_EN, plain_text(31 downto 16),
                                temp_block(31 downto 16),
                                block_half2);
    mux_right: mux2to1 port map(ENC_EN, plain_text(15 downto 0),
                                temp_block(15 downto 0), block_half1);

    reg16_left: reg16 port map (clk, reset, block_half2,
                                text_holder(31 downto 16));
    reg16_right: reg16 port map (clk, reset, block_half1,
                                text_holder(15 downto 0));

    cipher_text <= text_holder;

    round: round_cipher port map (text_holder, key_expanded, temp_block);

    keys: key_expansion port map (rnd, ENC_EN, key_word, clk, reset, key_expanded);
...
end;
```

SIMON Encryption in VHDL

Main Architecture Body

```
...
rnd_ctl: process(clk)
begin
  if (clk'event and clk= '1') then
    if (reset = '1') then
      rnd <= x"00";
      enc_run <= '0';
      done_flag <= '0';
    else
      if (rnd = x"1F") then
        rnd <= x"00";
        enc_run <= '0';
        done_flag <= '1';
      elsif (ENC_EN = '1' and enc_run = '0') then
        rnd <= x"00";
        enc_run <= '1';
      elsif (enc_run = '1') then
        rnd <= std_logic_vector(unsigned(rnd) + 1);
      else
        rnd <= x"00";
        done_flag <= '0';
        enc_run <= '0';
      end if;
    end if;
  end if;
end process;
...
```

A process is a type of
component bloc

Defined behaviorally

SIMON Encryption - Block Diagram

